

Khulna University of Engineering & Technology
B. Sc. Engineering Special Backlog Examination 2018
Department of Electrical and Electronic Engineering
EE 4223

High Voltage DC and Flexible AC Transmission

Time: 3 hours

Full Marks: 210

N.B.: (i) Answer **ANY THREE** questions from each section in separate scripts.

(ii) Figures in the right margin indicate full marks.

Section A

- Q1. (a) Compare AC and DC HV transmission system. What is break-even distance for HVDC transmission? (08)
- (b) Describe the applications of HVDC transmission. (07)
- (c) Show the different types of HVDC links with relevant circuit diagrams. Discuss the advantages and disadvantages of each. (12)
- (d) Explain the three HVDC link interconnection systems. (08)
- Q2. (a) Explain the construction and operation of a line commutated for HVDC. Deduce the equation for dc output voltage for 6-pulse converter. (12)
- (b) Draw the circuit arrangement of a six-pulse current source converter with no overlap. Deduce the equation for dc output voltage. Establish the relationship between dc and ac currents. (13)
- (c) Describe the operation of a line commutated converter for inverter operation. (10)
- Q3. (a) Describe the principle of operation of a shunt-active filter with net sketch of block diagram and proper waveforms. (15)
- (b) Draw the schematic diagram of half-bridge and full-bridge MMC cell. What is the significance of multi-level converter? (08)
- (c) A six-pulse HVDC converter is connected to 330 kV AC grid using a 330kV/220kV, 800MVA, $X_t = 12\%$ transformer. Determine the commutation overlap angle if the converter is operating at 20° firing angle and 1800A DC current. (12)
- Q4. (a) Mention the operating mode of VSC. How does a VSC act as an inverter and reactive power controller? Explain with proper vector diagrams. (10)
- (b) Sketch the circuit diagram of H-bridge type three level converter and explain the operation briefly. (10)
- (c) A single-phase VSC inverter has pure inductive load with $L = 21.5$ mH. The inverter operates in a square wave fashion with an AC frequency of 50 Hz and DC voltage of 200V. (15)
- (i) Express the instantaneous converter voltage and load current using the Fourier series.
- (ii) Calculate peak and RMS load current, and
- (iii) Calculate the power absorbed by load.

Section B

- Q5. (a) Explain the operating characteristic of a simple SVC circuit using TCR. (15)
- (b) Draw the pulse ratio modulated power measurement system. Draw and explain the operation of the IEEE Basic Model 2 for the SVC control system. (10)
- (c) Define ESCR and write down its equation. Explain operation of a SVC system with coupling capacitor. (10)
- Q6. (a) Describe the application of SVC in steady state and transient stability improvement. (12)
- (b) Explain the modes of TCSC operation. What are the requirements and advantages of TCSC? (11)
- (c) Describe the constant current and constant angle controls of TCSC based systems. Draw the block diagram and explain operation of constant current controlled TCSC system. (12)
- Q7. (a) Draw the schematic diagram of a STATCOM and explain its power circuit. Describe the real and reactive power control actions of a STATCOM. (13)
- (b) Deduce the steady state model of SATCOM using dc power in consideration. (12)
- (c) Explain the SSR mitigation technique using STATCOM. (10)
- Q8. (a) Explain the construction and operation of an SSSC. Show the power flow control of a SSSC. (12)
- (b) Draw the schematic diagram of a UPFC. Explain real and reactive power control aspects of the UPFC. (13)
- (c) Describe the application of UPFC in power flow control. (10)